

Chapter 37, Problem 2


[Return to Questions \(/admin/questions/0?sfield=magento_id&stext=0000027290&sdka=&stype=&sdiff=\)](/admin/questions/0?sfield=magento_id&stext=0000027290&sdka=&stype=&sdiff=)

Test Bank

Question preview

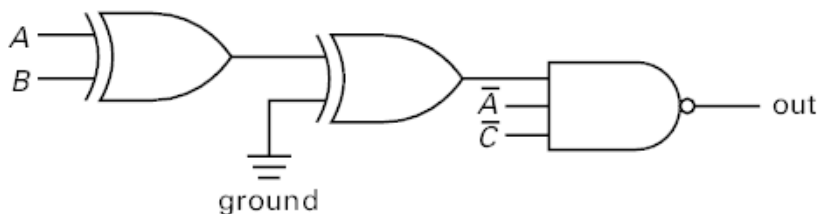Question

What is the output of the following logic circuit?



Answers

- (A) $A \cdot B \cdot C$
- (B) $A \cdot B \cdot C + A \cdot C$
- (C) $A \cdot B \cdot C + \bar{A} \cdot B \cdot C + A \cdot \bar{B} \cdot C + A \cdot B \cdot \bar{C}$
- (D) $A \cdot \bar{B} \cdot C$

The answer is (A).

Solution

Determine the Boolean logic expression from the logic circuit.

$$\text{out} = A \cdot C \cdot (\bar{0} + A \oplus \bar{B})$$

The logic "0" on the NOR gate makes the NOR gate effectively an inverter gate.

$$\overline{0 + A \oplus \bar{B}} = \overline{A \oplus \bar{B}}$$

The output is

$$\text{out} = A \cdot C \cdot (\overline{A \oplus \bar{B}})$$

The EXCLUSIVE-OR is equivalent to the conditions that will make the output true when the inputs are different.

$$A \oplus B = A \cdot \bar{B} + \bar{A} \cdot B$$

The negation of the EXCLUSIVE-OR is

$$\overline{A \oplus B} = \overline{A \cdot \bar{B} + \bar{A} \cdot B}$$

Apply De Morgan's theorem to the negation of the EXCLUSIVE-OR.

QUESTION DATA

Vendor

0000027290

Solving Time

<2

Difficulty

easy

Quantitative?

Yes

Status

Active

Created On

08/12/2019 09:38:30

PM

Published On

08/12/2019 09:38:30

PM

Modified On

08/12/2019 09:38:30

PM

OTHER VERSIONS

07/10/2018 11:42:37 P

(/admin/questions/prev

08/12/2019 09:38:30 P

(/admin/questions/prev

DISCIPLINES

FE Electrical and

Computer

(/admin/questions/inde

sfield=discipline&stext:

Electrical and Comput

KNOWLEDGE AREAS

Digital Systems

(/admin/questions/inde

sfield=area&stext=Digi

Systems)

PRODUCTS USED IN

FEEEPW

$$\begin{aligned}\overline{A \oplus B} &= \overline{A \cdot \overline{B} + \overline{A} \cdot B} = (\overline{A \cdot \overline{B}}) \cdot (\overline{\overline{A} \cdot B}) \\ &= (\overline{A} + B) \cdot (A + \overline{B})\end{aligned}$$

The AND is distributive over the OR, so the terms can be distributed analogously to cross multiplication in regular algebra.

$$\begin{aligned}\overline{A \oplus B} &= (\overline{A} + B) \cdot (A + \overline{B}) \\ &= A \cdot \overline{A} + A \cdot B + \overline{A} \cdot \overline{B} + B \cdot \overline{B} \\ &= 0 + A \cdot B + \overline{A} \cdot \overline{B} + 0 \\ &= A \cdot B + \overline{A} \cdot \overline{B}\end{aligned}$$

Substitute this result into the equation for the output and simplify.

$$\begin{aligned}\text{out} &= A \cdot C \cdot (\overline{A \oplus B}) \\ &= A \cdot C \cdot (A \cdot B + \overline{A} \cdot \overline{B}) \\ &= A \cdot C \cdot A \cdot B + A \cdot C \cdot \overline{A} \cdot \overline{B} \\ &= A \cdot A \cdot B \cdot C + A \cdot \overline{A} \cdot \overline{B} \cdot C \\ &= A \cdot B \cdot C + 0 \cdot \overline{B} \cdot C \\ &= A \cdot B \cdot C\end{aligned}$$

Chapter 16, Problem 1

[← Return to Questions \(/admin/questions/0?sfield=magento_id&stext=0000027338&sdka=&stype=&sdiff=\)](#)

Test Bank

Question preview

Question

A 9 V battery is connected across a semiconductor with a resistive diffused layer 1 cm wide, 10 cm long, and 1 cm thick. The diffused layer is doped with an n -type dopant to a concentration of 8.34×10^{17} carriers/cm³. The intrinsic carrier concentration in the diffused layer is 10^{10} carriers/cm³, the mobility of holes is $150 \text{ cm}^2/\text{V}\cdot\text{s}$, and the electron mobility is $360 \text{ cm}^2/\text{V}\cdot\text{s}$. Most nearly, what is the current through the diffused layer?

Answers

- (A) 0.12 A
- (B) 18 A
- (C) 43 A
- (D) 61 A

The answer is (C).

Solution

Use the law of mass action to find the hole concentration.

$$\begin{aligned} (p)(n) &= n_i^2 \\ p &= \frac{n_i^2}{n} = \frac{\left(1.0 \times 10^{10} \frac{\text{carriers}}{\text{cm}^3}\right)^2}{8.34 \times 10^{17} \frac{\text{carriers}}{\text{cm}^3}} \\ &= 1.20 \times 10^2 \text{ carriers/cm}^3 \end{aligned}$$

The conductivity of the semiconductor is

$$\begin{aligned} \sigma &= q(n\mu_n + p\mu_p) \\ &= (1.6 \times 10^{-19} \text{ C}) \left(\left(8.34 \times 10^{17} \frac{\text{carriers}}{\text{cm}^3}\right) \left(360 \frac{\text{cm}^2}{\text{V}\cdot\text{s}}\right) + \left(1.20 \times 10^2 \frac{\text{carriers}}{\text{cm}^3}\right) \left(150 \frac{\text{cm}^2}{\text{V}\cdot\text{s}}\right) \right) \\ &= 48.04 \text{ S/cm} \end{aligned}$$

Resistivity is the reciprocal of conductivity.

$$\begin{aligned} \rho &= \frac{1}{\sigma} = \frac{1}{48.04 \frac{\text{S}}{\text{cm}}} \\ &= 0.0208 \Omega\cdot\text{cm} \end{aligned}$$

QUESTION DATA

Vendor

0000027338

Solving Time

<2

Difficulty

easy

Quantitative?

Yes

Status

Active

Created On

07/10/2018 11:42:17

PM

Published On

07/10/2018 11:42:17

PM

Modified On

07/23/2019 05:16:44

PM

OTHER VERSIONS

07/10/2018 11:42:17 P

(/admin/questions/prev

DISCIPLINES

FE Other Disciplines
(/admin/questions/inde
sfield=discipline&stext:
Other Disciplines)

FE Electrical and
Computer
(/admin/questions/inde
sfield=discipline&stext:
Electrical and Comput

KNOWLEDGE AREAS

Basic Electrical
Engineering
(/admin/questions/inde
sfield=area&stext=Bas
Electrical Engineering)

The sheet resistance is

$$\begin{aligned}R_s &= \frac{\rho}{d} = \frac{0.0208 \Omega \cdot \text{cm}}{1 \text{ cm}} \\ &= 0.0208 \Omega \quad (\text{per square})\end{aligned}$$

The resistance of the diffused layer is

$$\begin{aligned}R &= R_s \left(\frac{L}{W} \right) = (0.0208 \Omega) \left(\frac{10 \text{ cm}}{1 \text{ cm}} \right) \\ &= 0.208 \Omega\end{aligned}$$

Use Ohm's law to find the current through the diffused layer.

$$\begin{aligned}V &= IR \\ I &= \frac{V}{R} = \frac{9 \text{ V}}{0.208 \Omega} \\ &= 43.3 \text{ A} \quad (43 \text{ A})\end{aligned}$$

Electronics
(/admin/questions/inde
sfield=area&stext=Elec

PRODUCTS USED IN
FEEPPW

Chapter 27, Problem 3

[Return to Questions \(/admin/questions/0?sfield=magento_id&stext=0000027423&sdka=&styp=&sdiff=\)](/admin/questions/0?sfield=magento_id&stext=0000027423&sdka=&styp=&sdiff=)

Test Bank Question

preview

Question

A lossless transmission line has a length of 30 m and a characteristic impedance of 50 Ω . The line operates at 5 MHz with a load impedance of 60 $\Omega + j40 \Omega$. The propagation constant is 1.396 rad/m. Most nearly, the input impedance seen by the source is

Answers

(A) 55.9 $\Omega \angle -31.0^\circ$ (B) 55.9 $\Omega \angle -35.7^\circ$ (C) 66.9 $\Omega \angle -35.7^\circ$ (D) 69.9 $\Omega \angle -33.2^\circ$ 

The answer is (C).

Solution

Use the equation for transmission line impedance at a point. The phase angle of the impedance at the source is

$$\beta d = \left(\left(1.396 \frac{\text{rad}}{\text{m}} \right) \left(\frac{180^\circ}{\pi} \right) \right) (30 \text{ m}) = 2400^\circ$$

The input impedance seen by the source is

$$\begin{aligned} \mathbf{Z}_{\text{in}}(d) &= \mathbf{Z}_0 \frac{\mathbf{Z}_L + j\mathbf{Z}_0 \tan(\beta d)}{\mathbf{Z}_0 + j\mathbf{Z}_L \tan(\beta d)} \\ &= (50 \Omega) \left(\frac{60 \Omega + j40 \Omega + (j50 \Omega) \tan 2400^\circ}{50 \Omega + (j60 \Omega - 40 \Omega) \tan 2400^\circ} \right) \\ &= (50 \Omega) \left(\frac{60 + j125}{-18 + j102} \right) \left(\frac{-18 - j102}{-18 - j102} \right) \\ &= (50 \Omega) \left(\frac{11,652 + j8370}{10,728} \right) \\ &= 54.3 \Omega + j39.01 \Omega \end{aligned}$$

Converting from rectangular form to polar form,

$$r = \sqrt{(54.3 \Omega)^2 + (39.01 \Omega)^2} = 66.86 \Omega$$

$$\theta = \arctan \frac{39.01 \Omega}{54.3 \Omega} = 35.69^\circ$$

$$\mathbf{Z}_{\text{in}}(d) = 66.86 \Omega \angle -35.69^\circ \quad (66.9 \Omega \angle -35.7^\circ)$$

QUESTION DATA

Vendor

0000027423

Solving Time

<2

Difficulty

easy

Quantitative?

Yes

Status

Active

Created On

07/10/2018 11:42:27 PM

Published On

07/10/2018 11:42:27 PM

Modified On

07/23/2019 05:16:55 PM

OTHER VERSIONS

07/10/2018 11:42:27 PM

(/admin/questions/previ

DISCIPLINES

FE Electrical and

Computer

(/admin/questions/inde

sfield=discipline&stext=

Electrical and Compute

KNOWLEDGE AREAS

Electromagnetics

(/admin/questions/inde

sfield=area&stext=Elec

PRODUCTS USED IN

FEEEPW

Chapter 8, Problem 3

[Return to Questions \(/admin/questions/0?sfield=magento_id&stext=0000087480&sdka=&stype=&sdiff=\)](/admin/questions/0?sfield=magento_id&stext=0000087480&sdka=&stype=&sdiff=)

Test Bank

Question preview

Question

What is the general solution to the following differential equation?

$$y'' + y' + y = 0$$

Answers

(A) $y = e^{-(1/2)x} \left(C_1 \cos \frac{\sqrt{3}}{2}x + C_2 \sin \frac{\sqrt{3}}{2}x \right)$

(B) $y = e^{-(1/2)x} \left(C_1 \cos \frac{3}{2}x + C_2 \sin \frac{3}{2}x \right)$

(C) $y = e^{-2x} \left(C_1 \cos \frac{\sqrt{3}}{2}x + C_2 \sin \frac{\sqrt{3}}{2}x \right)$

(D) $y = e^{-2x} \left(C_1 \cos \frac{3}{2}x + C_2 \sin \frac{3}{2}x \right)$

The answer is (A).

Solution

This is a second-order, homogeneous, linear differential equation with $a = b = 1$. This differential equation can be solved by the method of undetermined coefficients with a solution in the form $y = Ce^{rx}$. The substitution of the solution gives

$$(r^2 + ar + b) Ce^{rx} = 0$$

Because Ce^{rx} can never be zero, the characteristic equation is

$$r^2 + ar + b = 0$$

Because $a^2 = 1 < 4b = 4$, the general solution is in the form

$$y = e^{\alpha x} (C_1 \cos \beta x + C_2 \sin \beta x)$$

Then,

$$\alpha = -\frac{a}{2} = -1/2$$

$$\beta = \sqrt{\frac{4b - a^2}{2}} = \sqrt{\frac{(4)(1) - (1)^2}{2}} = \sqrt{3}/2$$

Therefore, the general solution is

$$y = e^{-(1/2)x} \left(C_1 \cos \frac{\sqrt{3}}{2}x + C_2 \sin \frac{\sqrt{3}}{2}x \right)$$

QUESTION DATA

Vendor

0000087480

Solving Time

Difficulty

easy

Quantitative?

No

Status

Active

Created On

12/18/2019 08:06:53

PM

Published On

12/18/2019 08:06:53

PM

Modified On

01/03/2020 08:32:42

PM

OTHER VERSIONS

05/11/2016 06:01:02 P

(/admin/questions/prev

03/27/2017 08:04:54 P

(/admin/questions/prev

03/08/2018 07:35:27 P

(/admin/questions/prev

05/23/2019 05:07:10 P

(/admin/questions/prev

07/23/2019 05:07:29 P

(/admin/questions/prev

09/16/2019 07:14:40 P

(/admin/questions/prev

12/18/2019 08:06:53 P

(/admin/questions/prev

DISCIPLINES

Chapter 37, Problem 1


[Return to Questions \(/admin/questions/0?sfield=magento_id&stext=0000089055&sdka=&stype=&sdiff=\)](/admin/questions/0?sfield=magento_id&stext=0000089055&sdka=&stype=&sdiff=)

Test Bank

Question preview

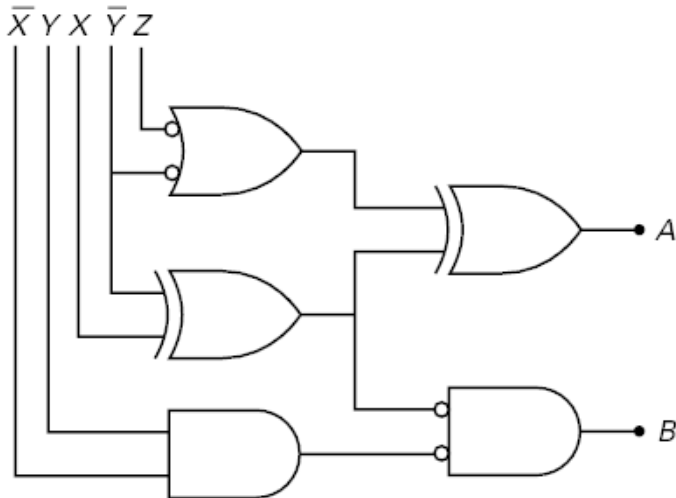Question

In the circuit shown, $X = 1$, $Y = 0$, and $Z = 1$.



What are the outputs, A and B ?

Answers

- (A) $A = 0, B = 0$
- (B) $A = 0, B = 1$
- (C) $A = 1, B = 0$
- (D) $A = 1, B = 1$

The answer is (B).

Solution

The NAND gate at the top left has inputs 1 and 1, so the condition is not satisfied and the output is 0.

The XOR gate at the middle left has inputs 1 and 1, so the condition is not satisfied and the output is 0.

The AND gate at the bottom left has inputs 0 and 0, so the condition is not satisfied and the output is 0.

The XOR gate at the top right has inputs 0 and 0, so the condition is not satisfied and the output is $A = 0$.

The NOR gate at the bottom right has inputs 0 and 0, so the condition is satisfied and the output is $B = 1$.

QUESTION DATA

Vendor

0000089055

Solving Time

<2

Difficulty

easy

Quantitative?

Yes

Status

Active

Created On

12/11/2017 04:50:01

PM

Published On

12/11/2017 04:50:01

PM

Modified On

07/23/2019 05:17:05

PM

OTHER VERSIONS

12/11/2017 04:50:01 P

(/admin/questions/prev

DISCIPLINES

FE Electrical and

Computer

(/admin/questions/inde

sfield=discipline&stext:

Electrical and Comput

KNOWLEDGE AREAS

Digital Systems

(/admin/questions/inde

sfield=area&stext=Digi

Systems)

PRODUCTS USED IN

FEEEPW

DSEE2W